

Analog Conventional Solution (ESE-2015 Test Series Dated 27.03.2015)


Sol.1 (a) $|V_T| = 1V$ $\text{unlox } \frac{W}{L} = 200 \mu A/V^2$
 $V_i = 5V$ $V_o = 2.5V$

For upper transistor: $V_{GS} = 5 - 2.5 = 2.5V$ so $V_{DS} = 10 - 2.5 = 7.5V$

\therefore Upper MOS is in saturation.


$I_D = k[V_{GS} - V_T]^2$ $I_D = 100 \times 10^{-6} [2.5 - 1]^2$ $I_D = 0.225 \text{ mA}$

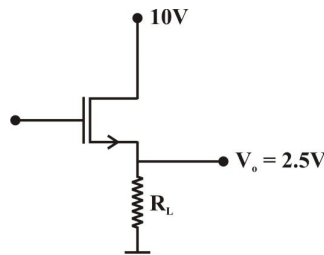Lower MOS is in triode region and behaving like a resistor and can be represented as follows:



$R_L = \frac{V_o}{I_D} = \frac{2.5}{0.225} = 1.11 \text{ K}$ **ANS**

Sol.1 (b) $v_i = 25 \sin \omega t$

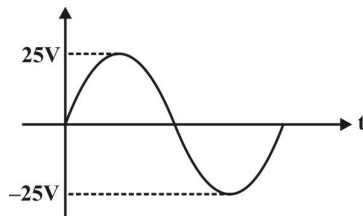

In +ve half; $D_1 \rightarrow$ forward biased

For $v_i > 15V$ $D_2 \rightarrow$ Breakdown region


Assuming ideal diodes $V_o = 15V$ for $v_i > 15V$ due to D_2


In -ve half; $D_1 \rightarrow$ Breakdown

$D_2 \rightarrow$ Forward biased


$v_o = -15V$ for $v_i < -15V$ due to D_1

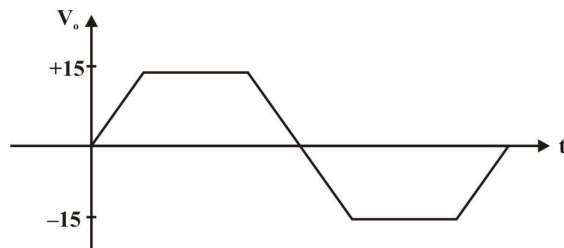For $-15 < v_i < 15V$; either D_1 or D_2 will be off. $\therefore v_o = v_i$ **ANS**



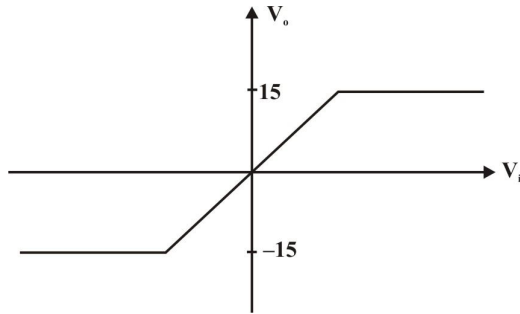

Sol. 1(c)

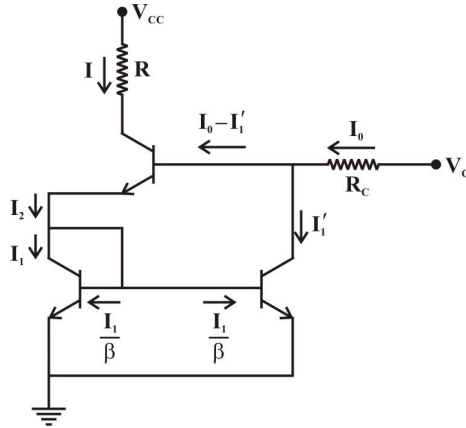

$$V_c = 5V \quad R_c = 2k\Omega \quad V_{CC} = 6V$$

$$R = 2.2k\Omega \quad V_{BE} = 0.7V \quad \beta = 100 \quad I = ?$$

By Current Mirror:

$$I_2 = I_1 \left(1 + \frac{2}{\beta} \right) \quad \text{--- (1)}$$

$$I + I_0 - I_1' = I_2$$

$$I = -I_0 + I_2 + I_1' = -I_0 + I_1 \left(1 + \frac{2}{\beta} \right) + I_1 \quad \text{--- (2)}$$

$$I = \beta(I_0 - I_1) \quad I_0 = \frac{I}{\beta} + I_1 \quad \text{--- (3)}$$

From (3)
$$I \left(1 + \frac{1}{\beta} \right) = -I_1 + I_1 \left(1 + \frac{2}{\beta} \right) + I_1 \left(\frac{\beta+1}{\beta} \right) I = I_1 \left(\frac{\beta+2}{\beta} \right)$$

$$I = I_1 \left(\frac{\beta+2}{\beta+1} \right) \quad \text{So} \quad I = \beta \left(I_0 - \left(\frac{\beta+1}{\beta+2} \right) I \right)$$

$$\frac{I}{\beta} = I_0 - \left(\frac{\beta+1}{\beta+2} \right) I \quad \Rightarrow \quad I \left[\frac{1}{\beta} + \frac{\beta+1}{\beta+2} \right] = I_0$$


$$\Rightarrow \quad I \left[\frac{\beta+2+\beta^2+\beta}{\beta(\beta+2)} \right] = I_0 \quad \Rightarrow \quad I = I_0 \left[\frac{\beta(\beta+2)}{\beta^2+2\beta+2} \right]$$

$$5 - 0 = I_0(2k) + 0.7 + 0.7 \quad \text{so} \quad I_0 = 1.8 \text{ mA}$$

$$I = 1.8 \left[\frac{(100)(102)}{100^2 + 200 + 2} \right] = \boxed{1.7996 \text{ mA} = I} \quad \text{ANS}$$

Sol. 1(d)

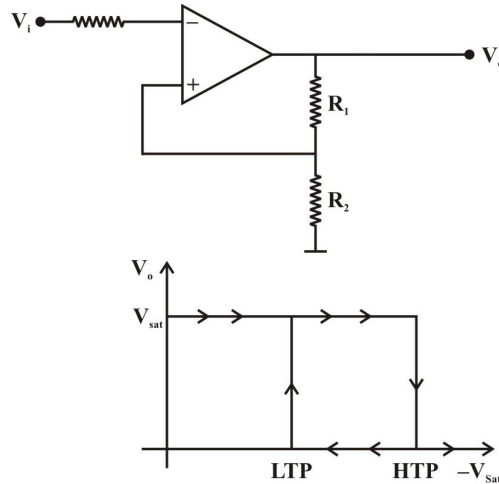Circuit for Schmitt trigger is as follows:



Hysteresis width (V_H) is $= UTP - LTP$.


If input noise is less than Hysteresis width then it can affect the performance of Schmitt trigger.

It is desirable phenomenon in case of Schmitt trigger.

Sol. 2(a)

$$V_o = 10V \quad I_o = 11 \text{ mA} \quad \frac{V_o}{V_i} = 10 \quad \frac{I_L}{I_i} = \infty \quad \text{ANS}$$

Sol.2 (b)

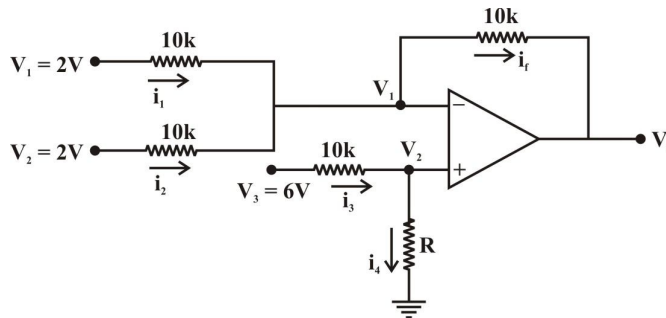

Because of virtual ground concept; $V_1 = V_2 = V$

Applying nodal analysis;

$$\frac{2 - V}{10k} + \frac{2 - V}{10k} = \frac{V - V_o}{10k}$$

$$4 - 2V = V - V_o \quad \text{--- (I)}$$

$$\frac{6 - V}{10k} = \frac{V}{R}$$

$$\frac{6 - V}{10k} = \frac{V}{R} \quad \text{--- (II)}$$

Output $V_o = 0V$ (Given)

From (I); $4 - 2V = V - 0 \quad V = \frac{4}{3}$

In eq. (II); $\frac{6 - \frac{4}{3}}{10k} = \frac{4}{3R} \Rightarrow \frac{14}{30k} = \frac{4}{3R}$

R = 2.85 K ANS

Sol. 2(c) Let $V_o = +V_{Sat} = 5V$

$V_p = V_{UTP} = \frac{5}{4} \times 1 = 1.25 V$

Charging: $V_c(\infty) = 5V \quad LTP = -2.5$

$V_c(0) = LTP = -2.5V$ So $V_c(t) = 1.25V$

$V_c(t) = V_c(\infty) + (V_c(0) - V_c(\infty))e^{-\Delta t_1/RC}$

$1.25 = 5 + (-2.5 - 5)e^{-\Delta t_1/RC} \quad e^{-\Delta t_1/RC} = 2$

Discharging:

$V_c(0) = 1.25 \quad V_c(\infty) = -5 \quad V_c(t) = -2.5$

$V_c(t) = V_c(\infty) + (V_c(0) - V_c(\infty))e^{-\Delta t_2/RC}$

$V_c(t) = -5 + (1.25 + 5)e^{-\Delta t_2/RC} = -2.5 \quad e^{-\Delta t_2/RC} = 2.5$

$e^{\frac{\Delta t_1 - \Delta t_2}{RC}} = \frac{2}{2.5} = 0.8$ **ANS**

Sol. 3(a) $A_C = \frac{h_{fe} R_C}{R_i + 2(1 + h_{fe})R_e} = 0.54$ **ANS**

$A_D = \frac{R_C}{2r_e} = \frac{47 I_E}{2V_T} = \frac{47 \times 75}{2 \times 20k} = 88.125$ **ANS**

$r_i = 2\beta r_e \quad r_e = \frac{r_i}{2\beta}$

Sol. 3(b) $A_d = \frac{R_c}{r_e} = \frac{R_c}{V_T} \times I_E$

$A_d \propto g_m \quad \text{So} \quad A_d \propto V_1$

$\frac{V_o}{V_i} = A_d \quad V_o = A_d V_2 \quad \boxed{V_o \propto V_1 \cdot V_2}$ **ANS**

Sol.3(c) Active load is an alternative of resistor because resistors are difficult to fabricate. It may be used as a constant current source in place of Emitter resistance. Constant current source has high value of internal resistance and value of Common Mode Gain will be decreased and CMRR value will be increased.

Sol. 4(a) Here $I_{REF} = I_c \left(1 + \frac{2}{\beta}\right)$

So
$$I_0 = \frac{I_{REF} \cdot \beta}{(\beta + 2)}$$


Here BJT current mirror circuit has finite output impedance $R_0 = \frac{V_A}{I_0} = 100\text{k}\Omega$

If finite β and R_0 is considered than

$$I_0 = \frac{I_{REF} \cdot \beta}{(\beta + 2)} \times \left(1 + \frac{V_0 - V_{BE}}{V_{Az}} \right) = 1.02 \text{ mA}$$

$$r_o = \frac{V_A}{I_c} = 100\text{K} \text{ ANS}$$

Sol.4 (b)

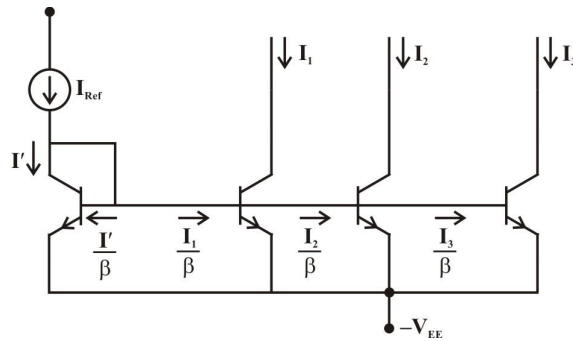

As all transistors are matched, collector currents will be same.

$$I' = I_1 = I_2 = I_3 = \dots = I_N$$

$$I_{ref} = \frac{I'}{\beta} + \frac{I_1}{\beta} + \frac{I_2}{\beta} + \frac{I_3}{\beta} + \dots + \frac{I_N}{\beta} + I'$$

$$I_{ref} = I' + \frac{(N+1)}{\beta} I'$$

$$I' = I_1 = \dots = I_N = \frac{I_{ref}}{1 + \frac{(N+1)}{\beta}}$$

If β is very large: $I' = I_1 = I_2 = \dots = I_N = I_{ref}$

For $\beta = 100$
$$I' = \frac{I_{ref}}{1 + \left(\frac{N+1}{100} \right)}$$

In ideal case of very large β :

$$I' = I_{ref} \quad \text{Error} = I_{ref} \left[1 - \frac{1}{1 + \left(\frac{N+1}{100} \right)} \right]$$

$$\% \text{ Error} = \frac{I_{\text{ref}} \left[\frac{\lambda + \left(\frac{N+1}{100} \right) - \lambda}{1 + \left(\frac{N+1}{100} \right)} \right]}{\frac{I_{\text{ref}}}{1 + \left(\frac{N+1}{100} \right)}} \times 100\% < 10$$

$$\frac{N+1}{10} < 0.1 \Rightarrow N = 9 \text{ ANS}$$

Sol.5 (a) without feed back $r_o = \frac{V_A}{I_c} = \frac{10}{1} = 10\text{k}\Omega \text{ ANS}$

In CE with feedback: $R_o = r_o + (1 + g_m r_o)(R_e \parallel r_\pi) = 177 \text{ Kohm} \text{ ANS}$

Sol.5 (b) $R_i = h_{ie} + (1 + \beta)R_e$

$$h_{ie} = \beta r_e = \frac{\beta V_T}{I_E}$$

$$I_C = 2.65 \text{ mA} \quad I_B = 0.0265 \text{ mA} \quad I_E = 2.6765 \text{ mA}$$

$$h_{ie} = 0.93 \text{ k}$$

$$R_i = 0.93 \text{ k} + (101)1 = 101.93 \text{ k} \text{ ANS}$$

Sol.6 (a) M_3 will be in saturation so

$$I_3 = K_3 (V_{GS_3} - V_t)^2 = \frac{20 - V_{GS_3}}{R_1} = 0.5874$$

M_1 will also be in saturation so

$$\frac{0.587}{2} = K_1 (V_{GS_1} - V_t)^2 \text{ So } V_{GS_1} = 2.71 \text{ Volt \& } R_1 = 30 \text{ K} \text{ ANS}$$

Sol.6 (b) $A = -2000 \quad \beta = \frac{1}{150} \quad h_{fe} = 200$

$$h_{ie} = 2 \text{ k} \quad V_{o1} = -h_{fe} i_b R_c$$

$$i_{o1} = \frac{V_s - V_f}{R_s + h_{ie}}$$

$$V_{o1} = V_i = -\frac{h_{fe} R_c}{(R_s + h_{ie})} (V_s - V_f) = -\frac{200 \times 3 \text{ k}}{3 \text{ k}} (V_s - V_f) = -200(V_s - V_f)$$

$$V_f = \beta V_o \quad \frac{V_o}{V_i} = -200$$

So $V_i = -200 V_s + 200 \beta V_o \quad \frac{V_o}{V_s} = 149.9 \text{ ANS}$